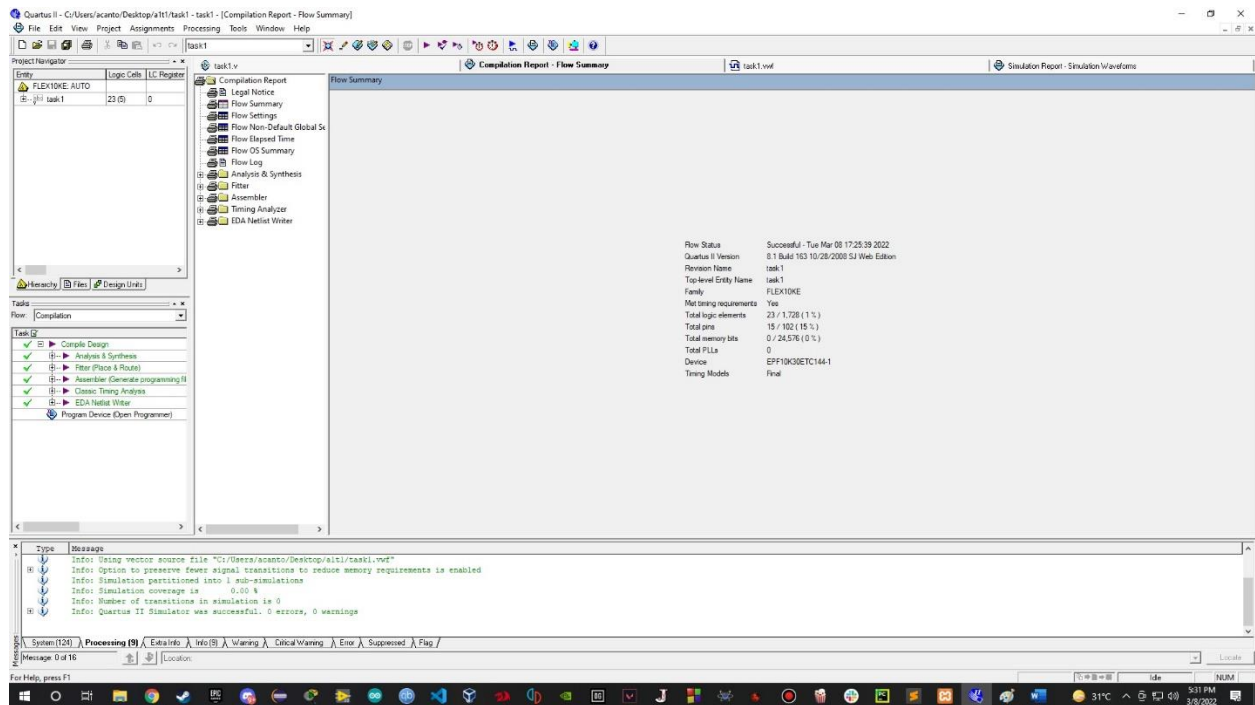



Task1:**Code:**

```
module task1(A,B,Cin,Result,Cout,add_sub);  
    output [3:0] Result;  
    output Cout;  
  
    reg [3:0] Result;  
    reg Cout;  
    reg [4:0] temp;  
  
    input add_sub, Cin;  
    input [3:0] A, B;  
  
    wire add_sub;  
  
    always@(add_sub or A or B or Cin)  
    begin  
        if (add_sub == 1)  
            temp = A + B + Cin;  
            Result = temp [3:0];  
            Cout = temp[4];  
        if (add_sub == 0)  
            temp = A - B - Cin;  
            Result = temp [3:0];  
            Cout = temp[4];  
        end  
    endmodule
```

Compilation Report:



simulation report:

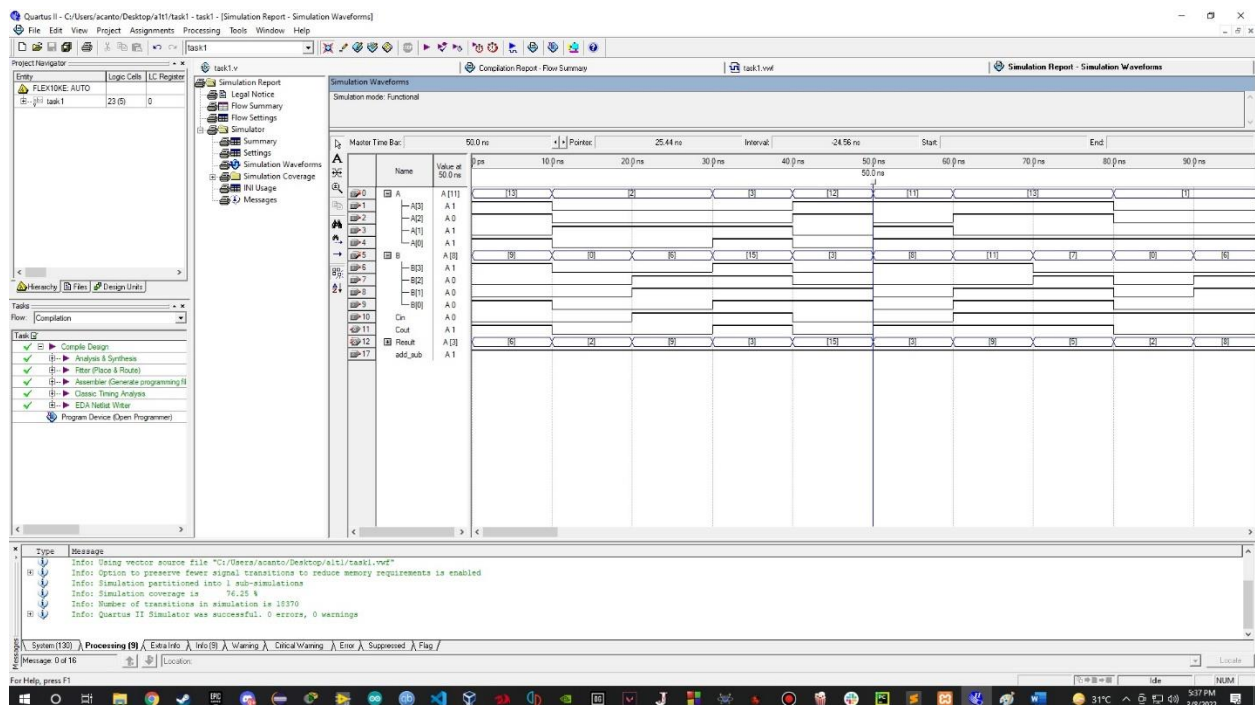

Discussion: Here this is a 4-bit full adder/subtractor. It works as both adder and subtractor. There is a control pin named add_sub which will control the functionality of the system. There is a carry in pin which is for the extra bit in the LSB. And the carry out pin shows extra bit of the addition of A and B. for example in the above picture the value of A is 11 and value of B is 8 so

the addition is 19. But as it is a 5 bit output so the output generates 1 in carry out and 0011 in result. So the total output is 10011 which is in decimal 19.

Task 2:


Code:

```
module task2(A, Y);


    input [3:0]Y;
    output reg [1:0]A;

    always@(Y)
    begin
        casex(Y)
            4'bxxx1:A = 2'b00;
            4'bxx1x:A = 2'b01;
            4'b1xxx:A = 2'b11;
            4'bx1xx:A = 2'b10;
        endcase
    end
endmodule
```

compilation report:

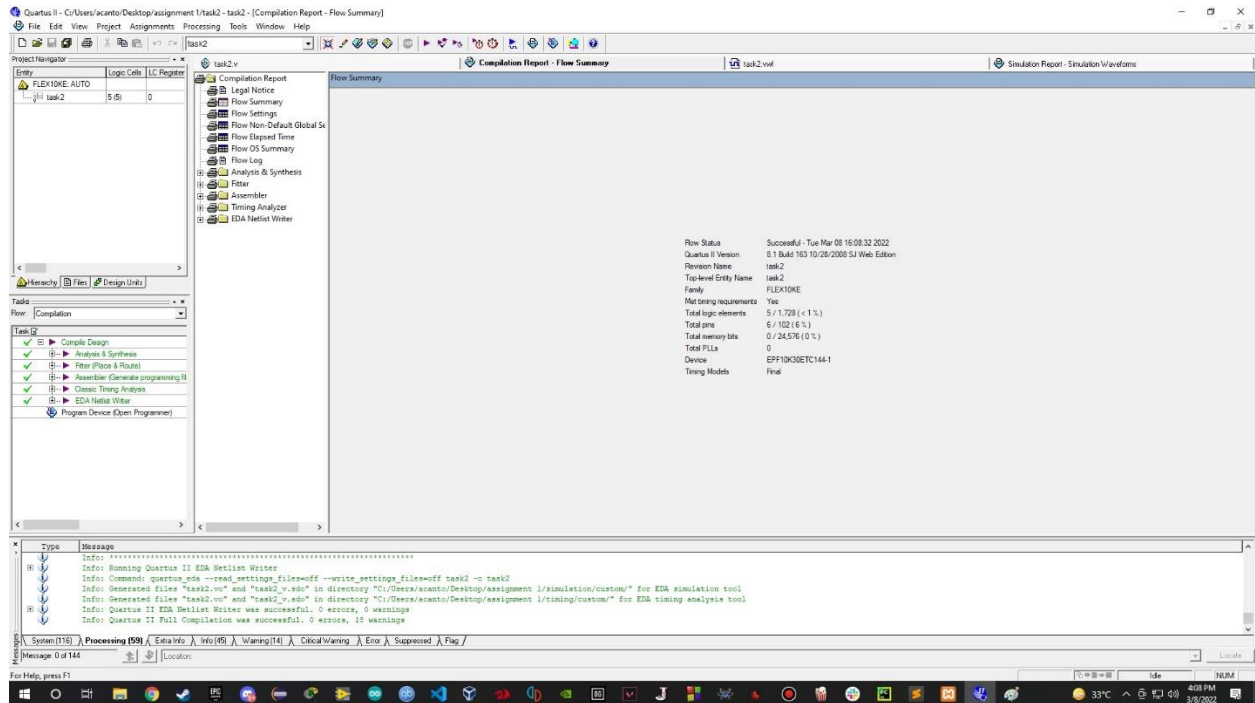

simulation report:

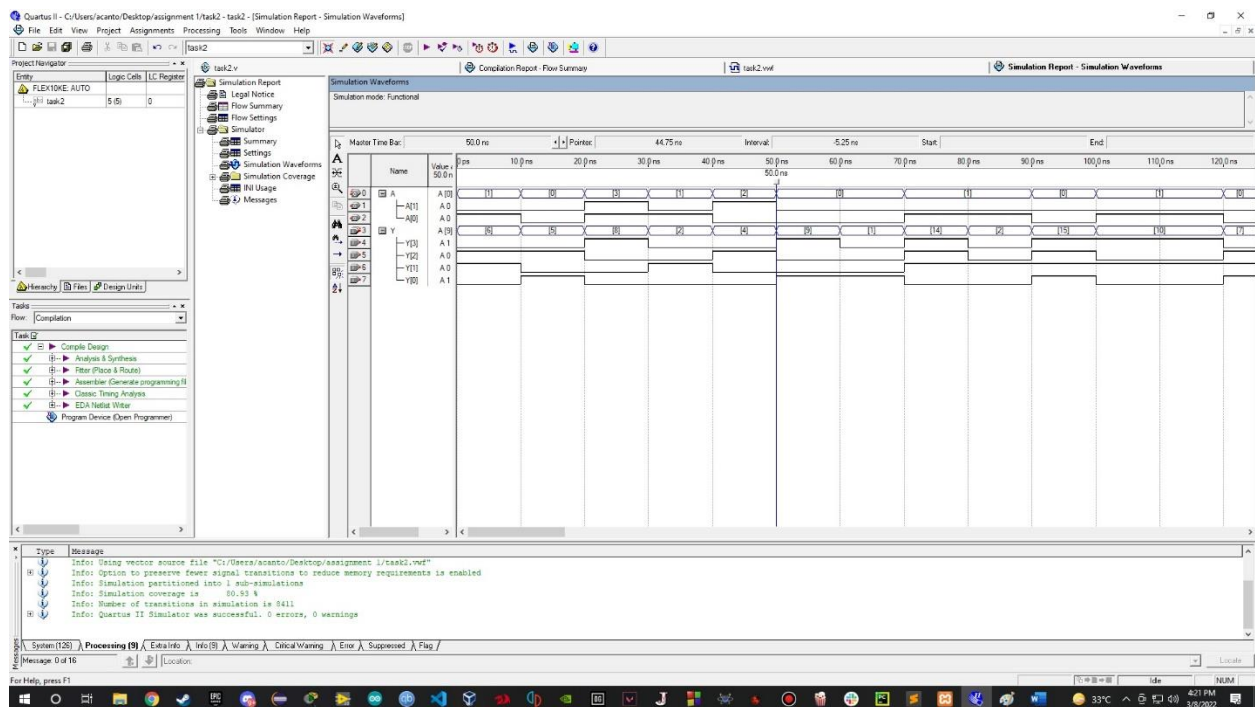

Discussion: Since this is a priority encoder, and according to the question the priority is $0 > 1 > 3 > 2$. So, if bit 0 gets 1; the output will show 0 as here 0 is the highest priority. We get output 1 if bit 1 is 1. Again, we get output 3 if bit 3 is 1. Finally, we will get output 2 if all bits are 0 and only bit 2 is 1 as bit 2 has the lowest priority. And if multiple bits or all bit is high then

the output will be 0 as 0 has the highest priority. So, if multiple bits are high then the system will generate output as the priority sequence.